

# Digital Bubble Level - Cell Layout

Vladislav Pomogaev - 26951160

December 5, 2021

## 1 Introduction

This device forms a digital bubble level; also called a spirit level. It can be helpful in levelling things horizontally. The project began as a synthesised set of Verilog files for the Efinix XylonI FPGA development board, but I have since extracted the core FSM from that project, laid it out with the 45nm standard cell library, and verified its operation though simulations.

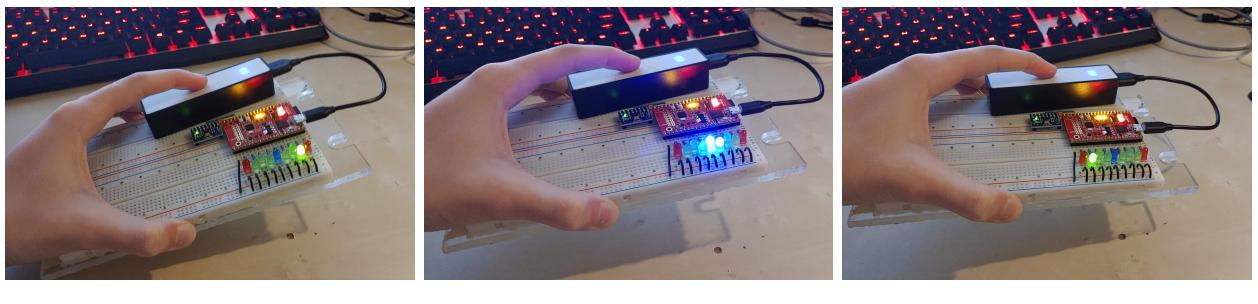


Figure 1: Photo stills of the original device in action. When you tilt the device to the left as in a), the LEDs to the right light up. As you tilt the device more to the right, the lit LED moves from right to left as in b) and c). When level, the blue center LED lights up.

## 2 Overview

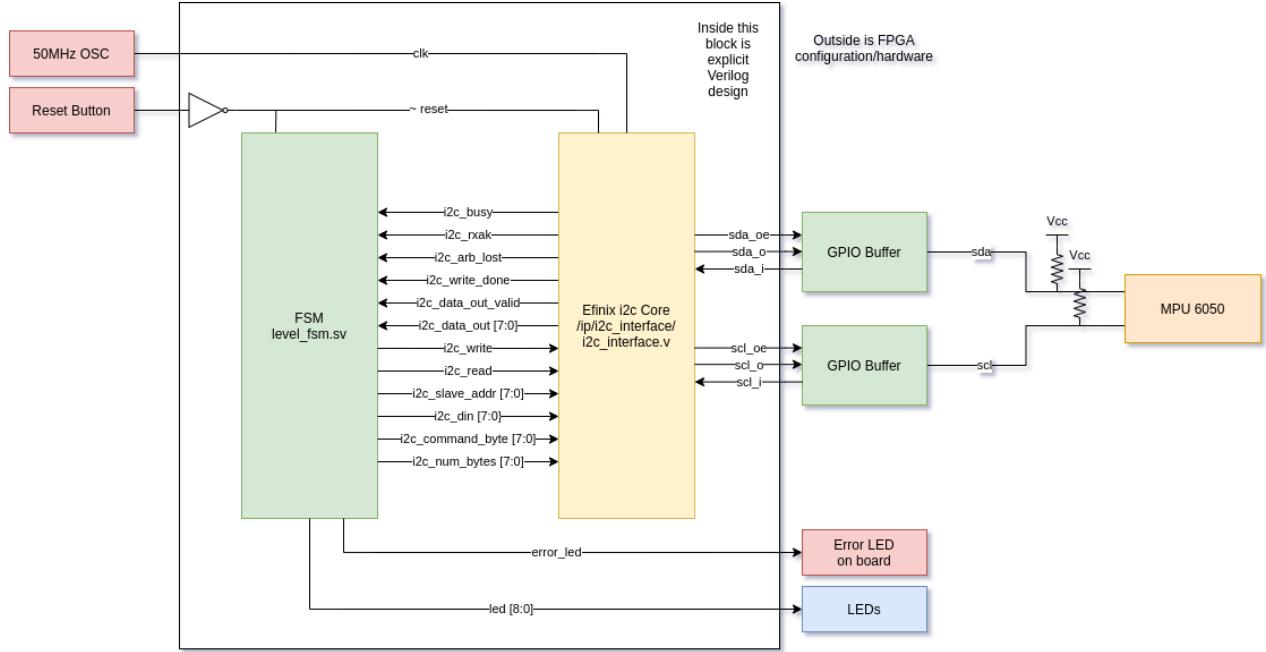


Figure 2: Block diagram of the FSM and how it forms the bubble-level system. The level FSM talks to the I2C core, which communicates to the MPU via a set of buffered GPIO blocks on the FPGA. A reset button resets all FSMs to their initial state. The design runs is compiled for a 50MHz clock constraint. The output to outside of the FPGA is buffered through the GPIO logic blocks, which was the reason I used IP specific to the FPGA. I only did the layout and verification for the level\_fsm.sv file from the original project.

### 2.1 Ports

Port	Width (bits)	Interface	Direction	Description
clk_i	1	System	Input	Clock input. 50MHz max.
reset_i	1	System	Input	Active high reset input
i2c_busy_i	1	I2C	Input	Logic high indicates that the I2C bus is busy.
i2c_rxak_i	1	I2C	Input	Logic low indicates that the I2C slave device received and acknowledged the I2C transfer
i2c_arb_lost_i	1	I2C	Input	Logic high indicated there is arbitration lost in the I2C transfer
i2c_write_done_i	1	I2C	Input	Logic high indicates that I2C master write data is sent and ready to accept by I2C slave device.
i2c_data_out_valid_i	1	I2C	Input	Logic high indicates that I2C master read data is valid and ready to read by user.
i2c_data_out_i	8	I2C	Input	Data read input port
i2c_write_o	1	I2C	Output	Write to slave strobe high
i2c_read_o	1	I2C	Output	Read from slave strobe high
i2c_slave_addr_o	8	I2C	Output	Address of slave in 8bit format. Add trailing zero to use 7-bit addressing.
i2c_din_o	8	I2C	Output	Data read from slave
i2c_command_byte_o	8	I2C	Output	Command byte sent to slave. (Register to read from)
i2c_num_bytes_o	8	I2C	Output	Number of bytes of data to write or read. Includes the command byte (if sending one byte, i2c_num_bytes.o = 'd2)
error_led_o	1	System	Output	Active high if an error has occurred in state machine; lost bytes, error writing to slave or reading. Reset FSM to try again.
led_o	9	System	Output	LED array output of bubble level

### 3 Standard Library Layout

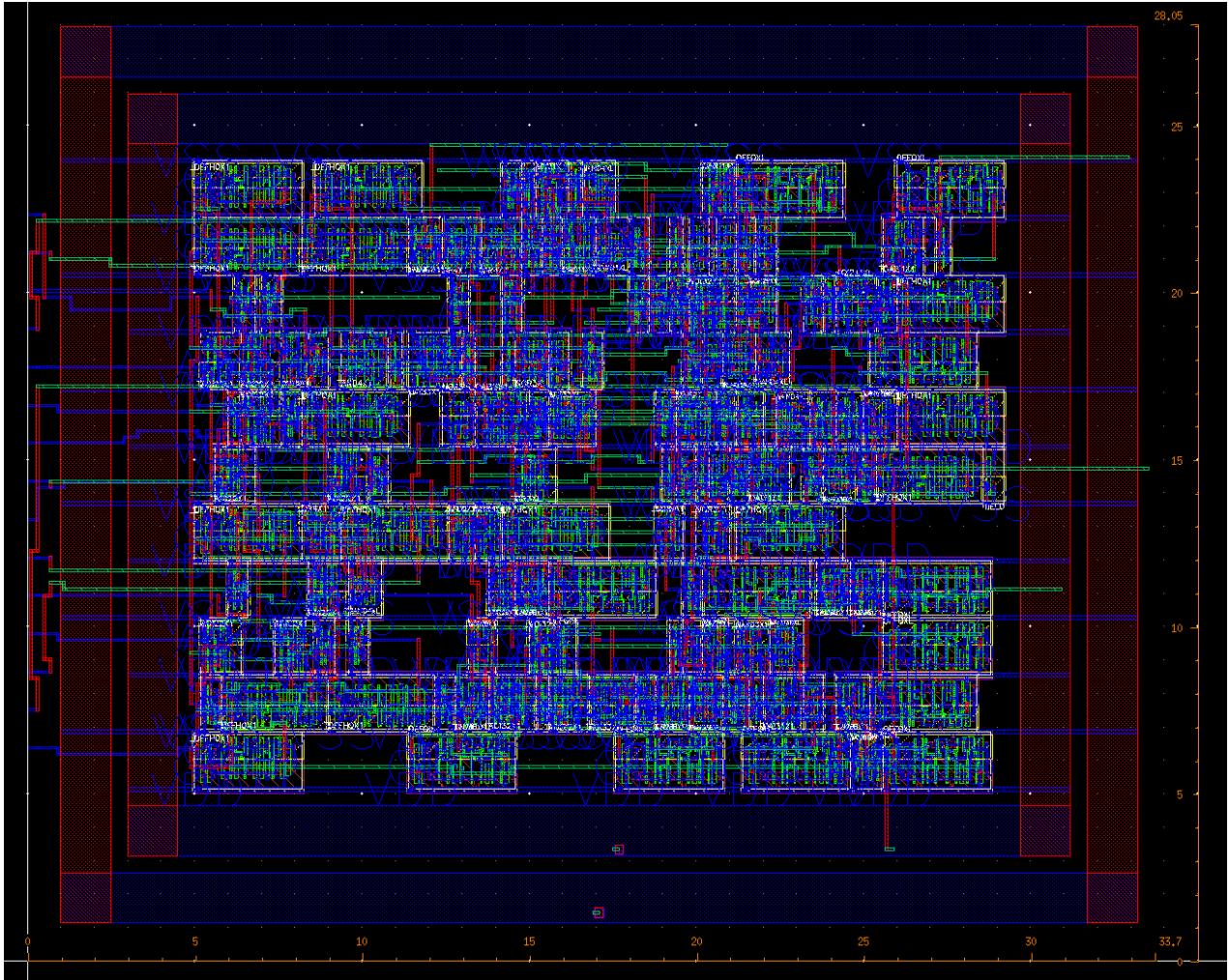


Figure 3: The level\_fsm.sv file was synthesized and laid out using the 45nm standard cell library provided. The ports were aligned as such: inputs on the left, outputs on the right, and power on the bottom. The very outer dimensions are 33um x 28um, for a total area of 924um $\hat{2}$ .

## 4 Simulation/Verification

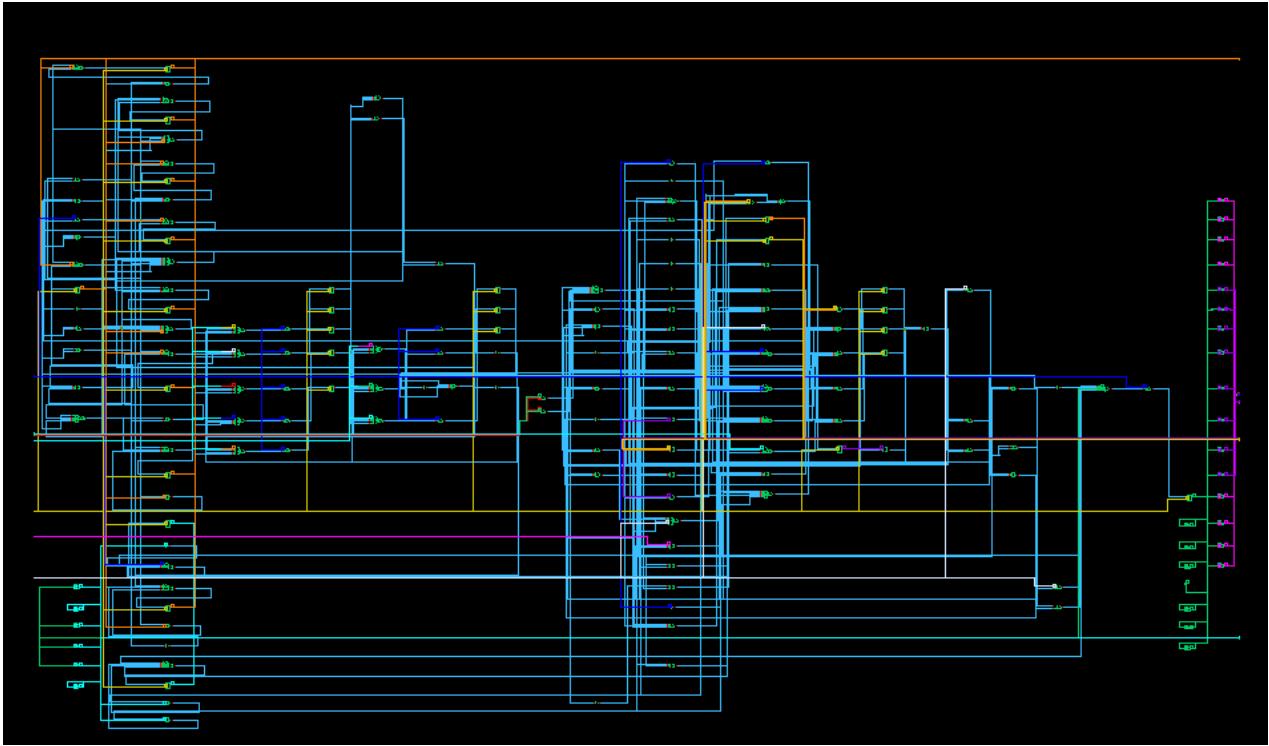


Figure 4: The Verilog file was also translated to a RTL layout and displayed in viewable form. Here we see the entire FSM schematic in terms of logic gates.

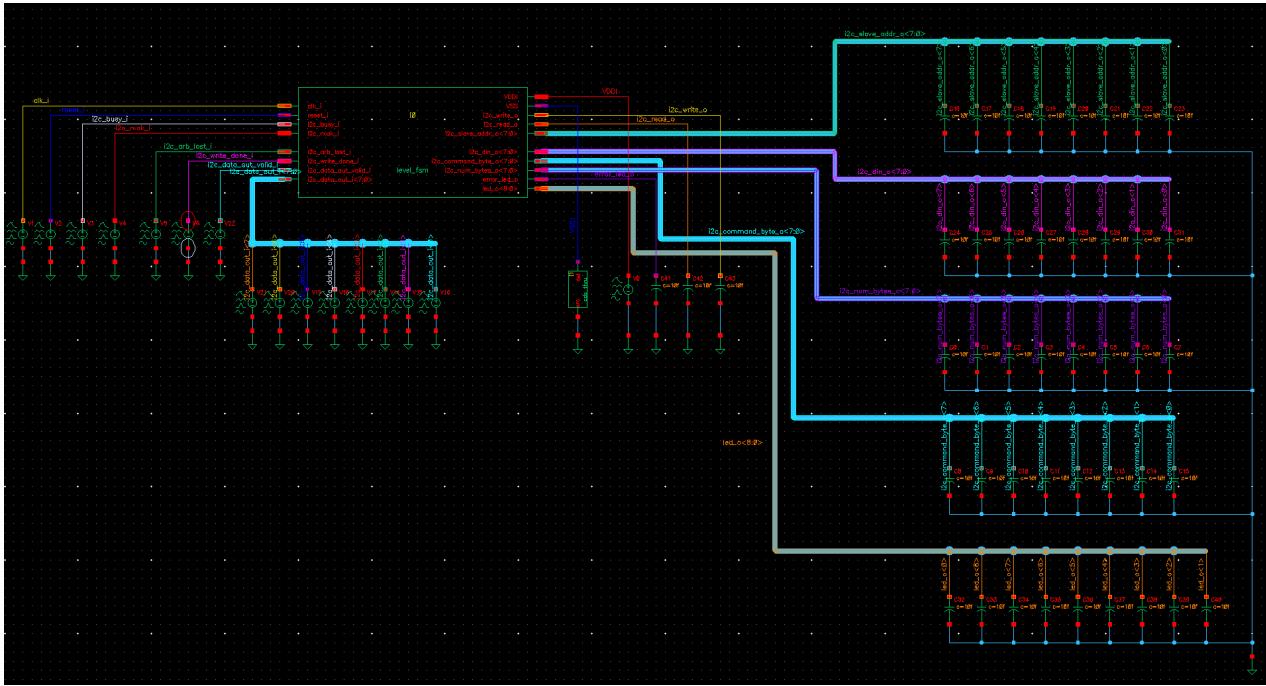


Figure 5: The previous RTL design was transformed into a new cell view. This cell view was placed in a test-bench schematic. Each output of the FSM was loaded with a 10fF capacitor. An array of 1V supplies was used to drive the input signals.

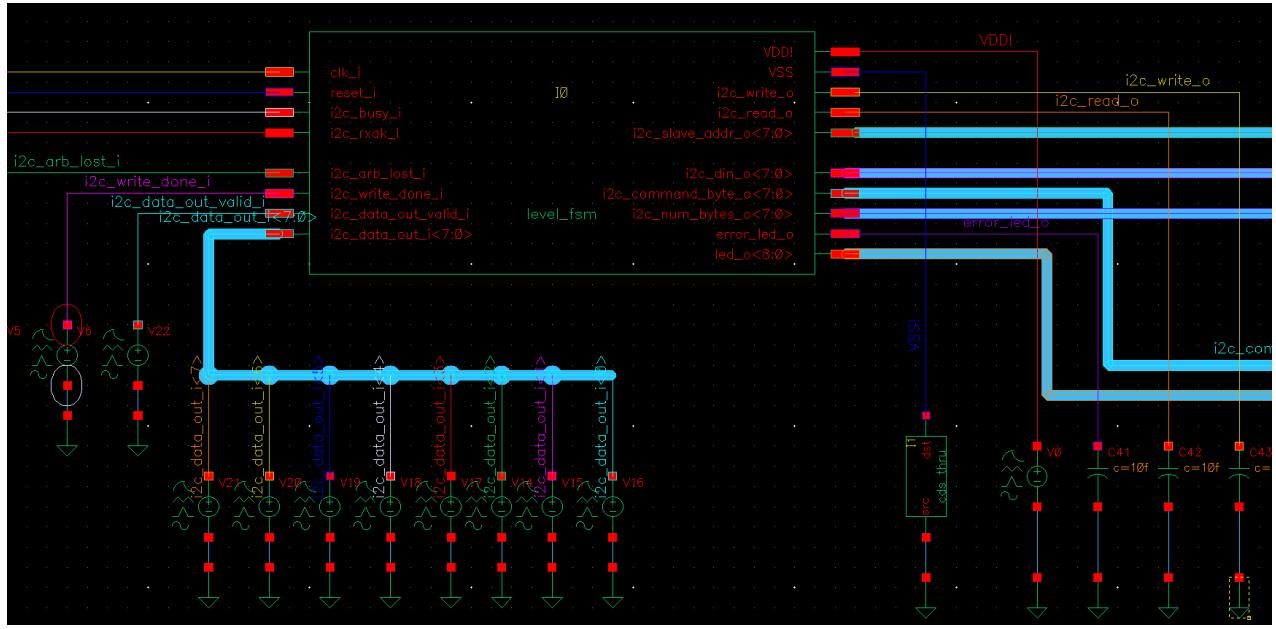


Figure 6: Here is a closeup of the test-bench schematic. The voltage input signals were set up manually using an array of input voltage levels that corresponded to the input vectors used in the original Verilog test bench.

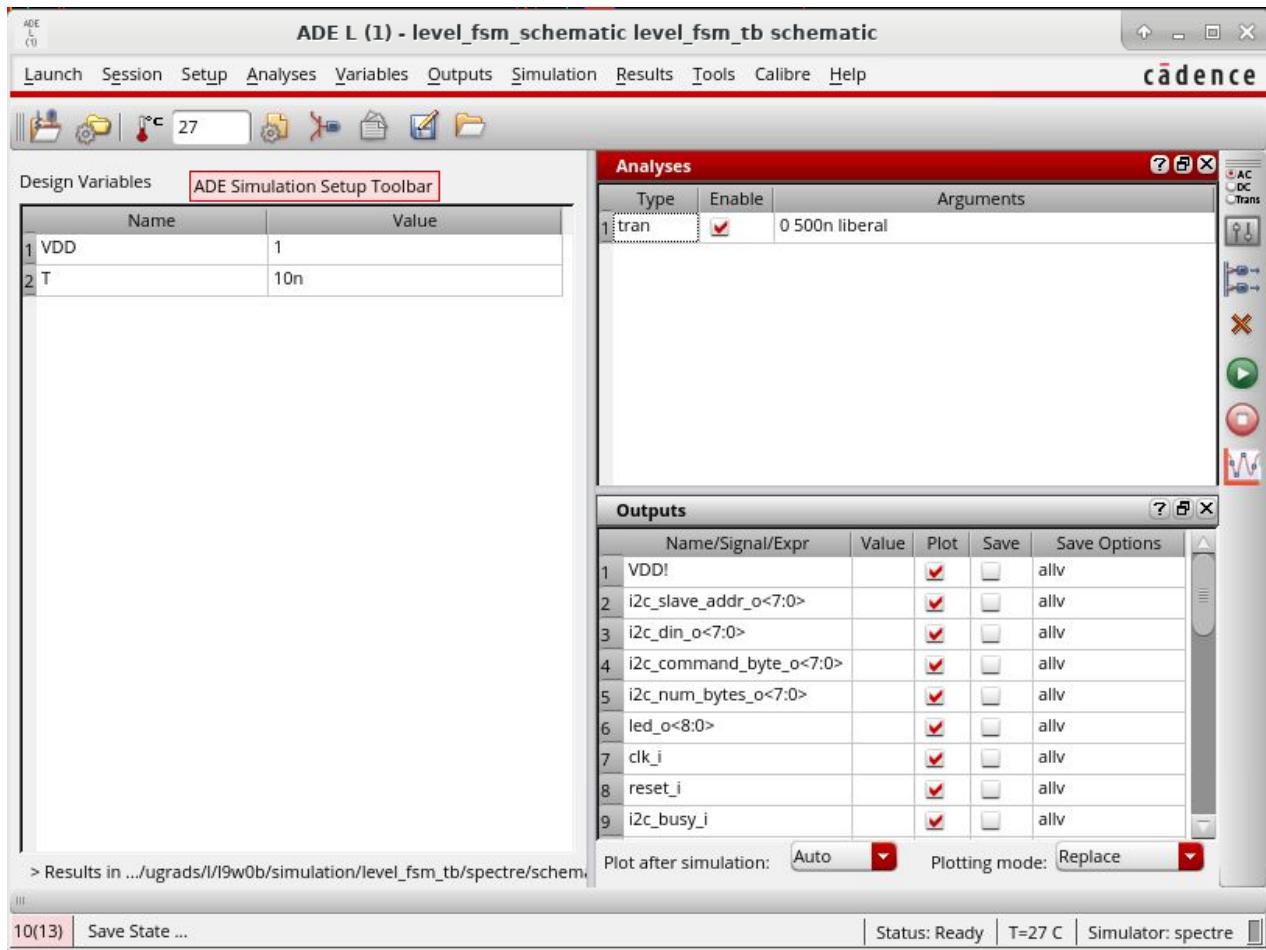


Figure 7: The simulation was set up using ADE. The simulation duration was the same length as the original Verilog test bench file.



Figure 8: For comparison, here is the input and output vector of the original Verilog simulation. This simulation tests does the following in this order: 1) FSM reset 2) Write to accelerometer to wake it up 3) Wait for valid response 4) Read from accelerometer register 5) Display level on LEDs. 6) Read from accelerometer register, but this time receive an error 7) Verify error\_led output 8) Reset FSM 9) Write to accelerometer to wake it up, but this time receive an error 10) Verify error\_led output 11) Stall forever. This procedure tests an overwhelming majority of the FSM. Signals have been color-coded for your convenience.

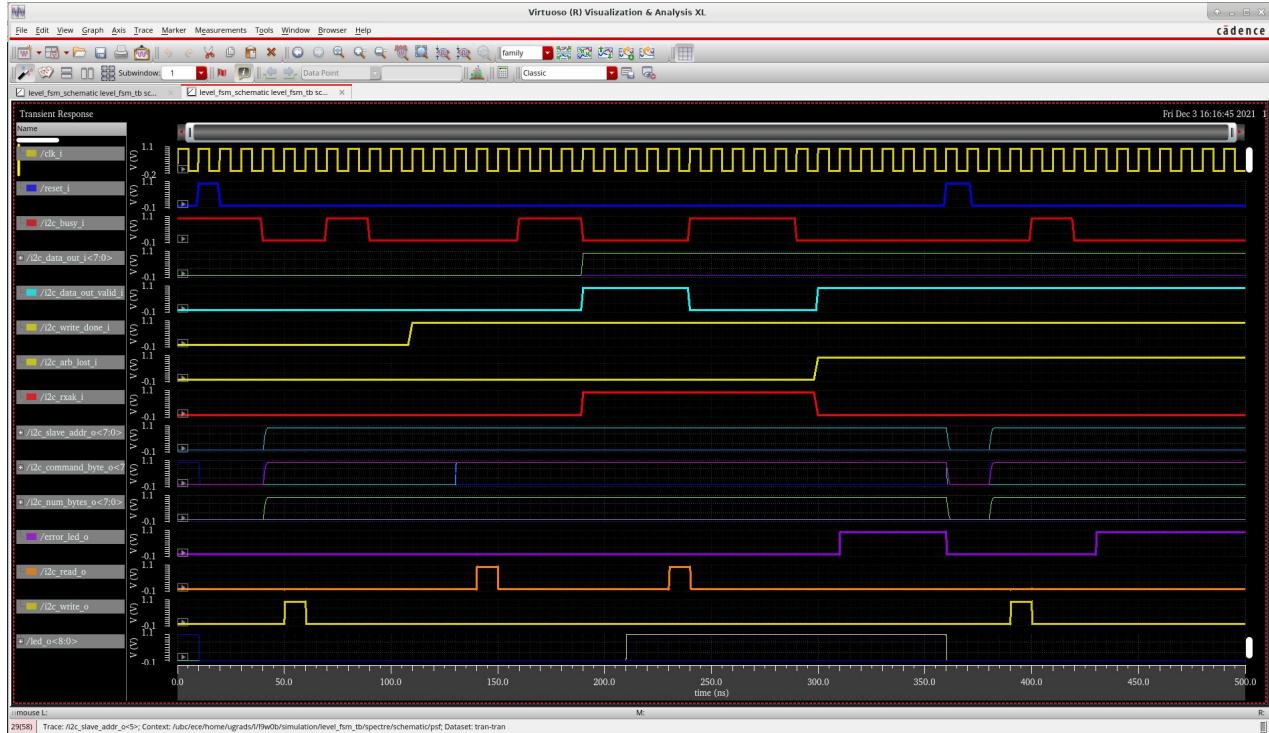


Figure 9: Here is the same test bench but now it is executed in Virtuoso. As we can see the waveforms are the same, but we see characteristic RC delays.



Figure 10: Blah blah blah

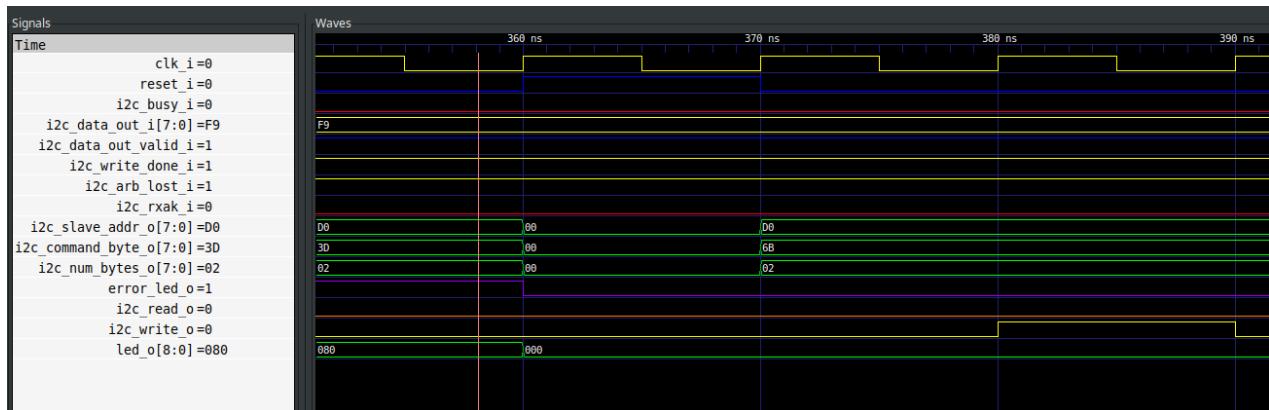


Figure 11: Blah blah blah

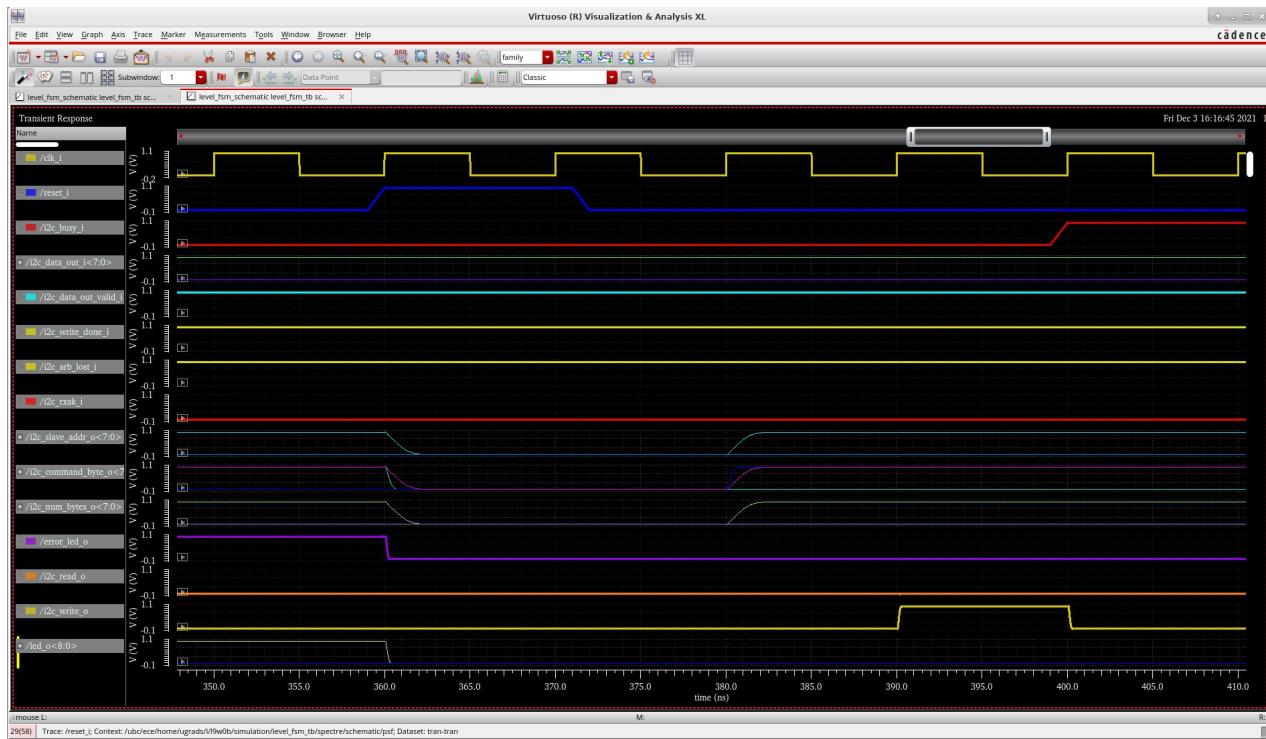


Figure 12: Blah blah blah


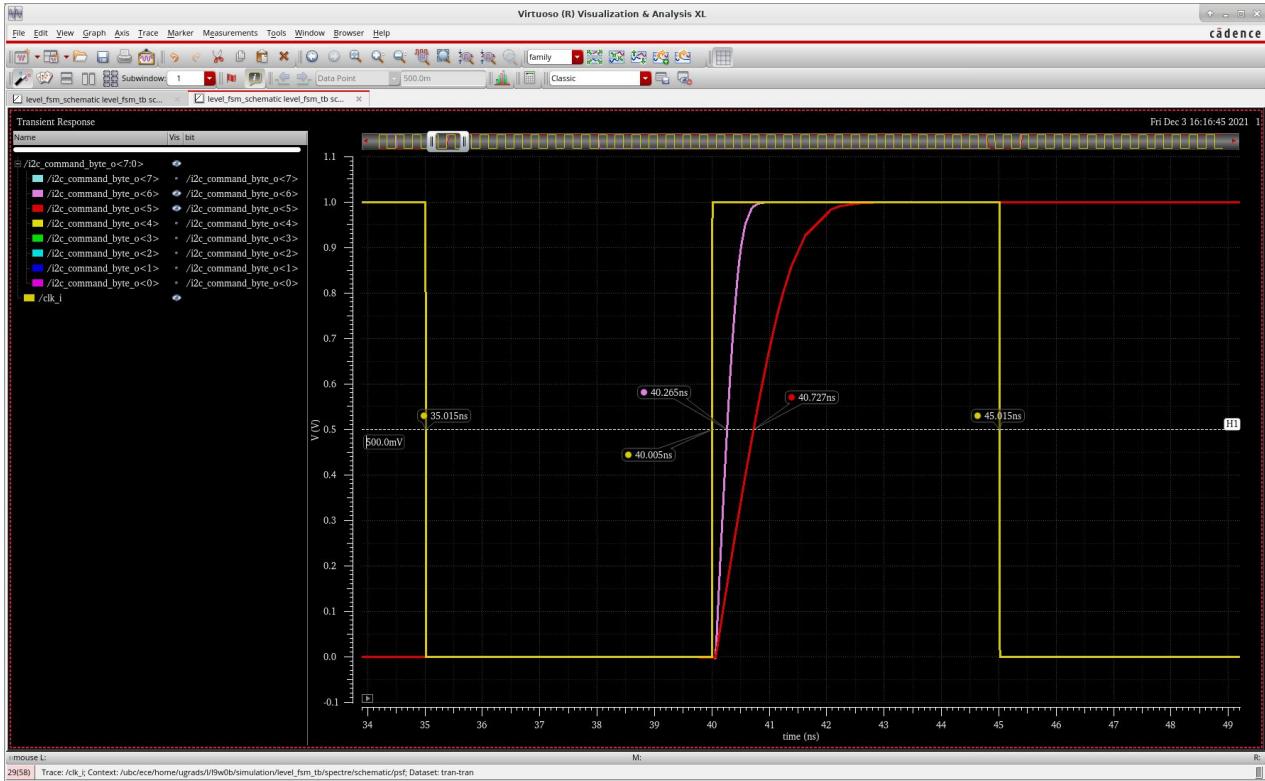


Figure 13: Blah blah blah

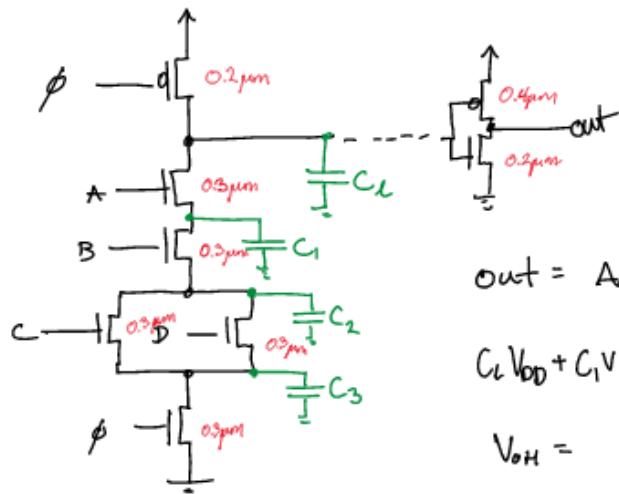

## 5 Written Questions

2)




$$out = AB(C+D)$$

$$C_L V_{DD} + C_1 V_1 + C_2 V_2 = (C_L + C_1 + C_2) V_{OH}$$

$$V_{OH} = \frac{C_L V_{DD} + C_1 V_1 + C_2 V_2}{C_L + C_1 + C_2}$$

for max reduction in  $V_{OH}$ ,  $V_{1,i} = V_{2,i} = 0V$

worst case scenario:

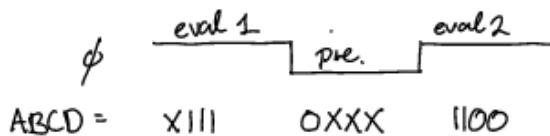

$$\begin{aligned} C_L &= (0.5\mu m)(1.7\mu m) + (0.6\mu m)(2.7\mu m) \\ &= 0.5fF + 1.2fF \\ &= 1.7fF \end{aligned}$$

$$\begin{aligned} C_1 &= 0.6\mu m \times 1fF/\mu m \\ &= 0.6fF \end{aligned}$$

$$\begin{aligned} C_2 &= 0.9\mu m \times 1fF/\mu m \\ &= 0.9fF \end{aligned}$$

I'm assuming  
no source/drain  
sharing here.

Charge sharing voltage reduction %


$$\frac{V_{OH} \times 100\%}{V_{DD}} = \frac{C_L \times 100\%}{C_L + C_1 + C_2} = \frac{1.7 \times 100\%}{1.7 + 0.6 + 0.9} = \frac{1.7 \times 100\%}{3.2} = 53\%$$

$$C_L = 1.7fF$$

$$C_1 = 0.6fF$$

$$C_2 = 0.9fF$$

3)

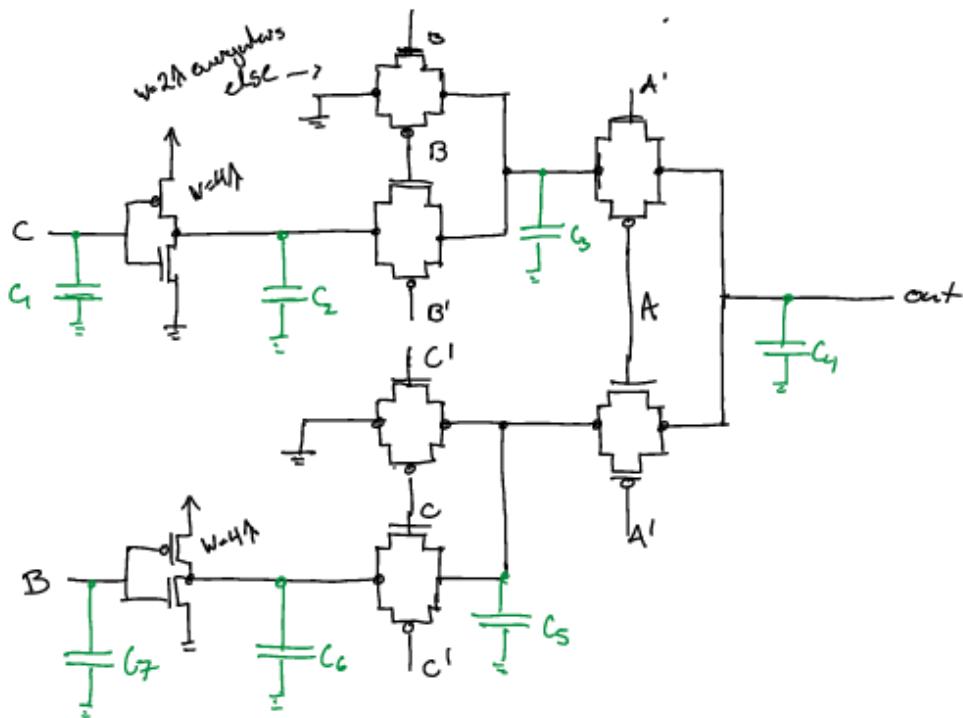

$$C_1 = 6A \times C_g$$

$$C_2 = 6A \times C_{eff} + 4A C_{eff} + B \cdot (2A C_g)$$

$$C_3 = 4A C_{eff} + B(2A C_g) + 4A C_{eff} + B'(2A C_g) + 4A C_{eff} + A'(2A C_g)$$

$$= 12A C_{eff} + 2A C_g + A'(2A C_g)$$

$$C_4 = A(2A C_g) + A'(2A C_g) + 8A C_{eff}$$


$$= 8A C_{eff} + 2A C_g$$

$$C_5 = 12A C_{eff} + C(2A C_g) + C'(2A C_g) + A(2A C_g)$$

$$= 12A C_{eff} + 2A C_g + A(2A C_g)$$


$$C_6 = 10A C_{eff} + C(2A C_g)$$

$$C_7 = 6A C_g$$

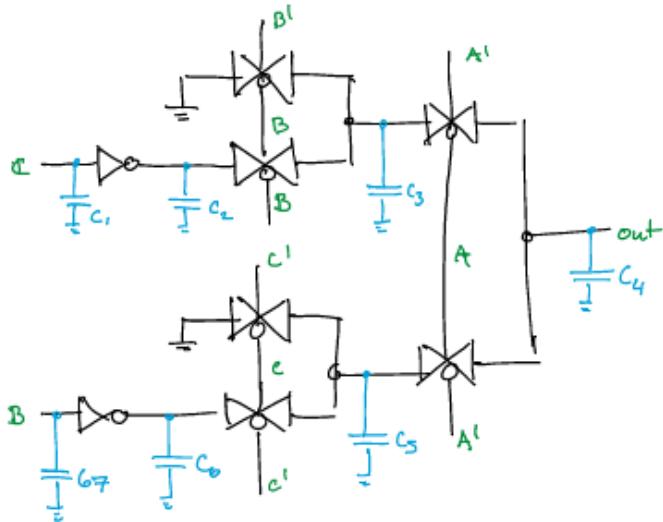

$$out = \bar{C}BA' + \bar{B}CA$$

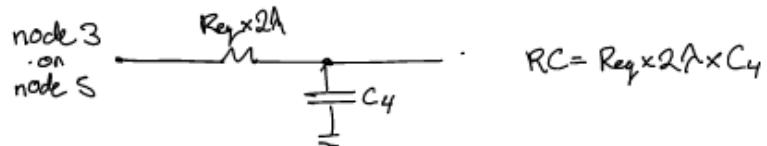For minimum delay I will assume we can use almost delay and ignore charged capacitors.




$$RC = \tau \approx Req \times 2A \times (8C_{eff} + 2AC_g)$$

$$\text{assuming: } Req = 12.5k/\square \quad C_{eff} = 1PF/\mu m \\ \lambda = 0.1\mu m \quad C_g = 2fF/\mu m$$

$$\tau \approx 12.5k \times 2 \times 0.1\mu m \times (8 \times 0.1 \times 1P + 2 \times 0.1 \times 2f) \\ \approx 12 \text{ ps}$$

longest delay:

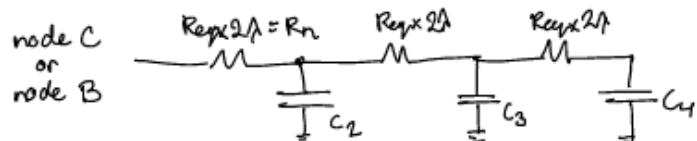

$$RC \approx \tau = Rn(C_2 + C_3 + C_4) + 2Rn(C_3 + C_4) + 3Rn(C_4)$$

$$= Rn [C_2 + 3C_3 + 6C_4]$$

$$= Req \times 2A \cdot [10A'G_{eff} + B2AG_g + 36A'G_{eff} + 6AG_g + A'GA'G_g + 48A'G_{eff} + 12AG_g]$$

$$= Rn \times 2A [94A'G_{eff} + 96AG_g]$$

Q5)

$$\alpha = 1$$



$$\alpha = 0.2$$

